

Power Transmission

Homework 6

Brett Roberts

5.2

A 200-km, 230-kV, 60-Hz, three-phase line has a positive-sequence series impedance $z = 0.08 + j0.48 \Omega/\text{km}$ and a positive-sequence shunt admittance $y = j3.33 \times 10^{-6} \text{ S/km}$. At full load, the line delivers 250 MW at 0.99 p.f. lagging and at 220 kV. Using the nominal π circuit, calculate: (a) the ABCD parameters, (b) the sending-end voltage and current, and (c) the percent voltage regulation.

(a)

$$\begin{aligned}
 \rightarrow Z &= (z)(l) = (0.08 + j0.48)(200) = 16 + j96 \Omega = 97.33 \angle 80.54^\circ \Omega \\
 \rightarrow Y &= (y)(l) = (j3.33 \cdot 10^{-6})(200) = j6.66 \cdot 10^{-4} \text{ S} = 6.66 \cdot 10^{-4} \angle 90^\circ \text{ S} \\
 \rightarrow A = D &= 1 + \frac{YZ}{2} = 1 + \frac{(16 + j96)(j6.66 \cdot 10^{-4})}{2} = \boxed{0.9681 \angle 0.317^\circ} \\
 \rightarrow B = Z &= \boxed{16 + j96 \Omega} \\
 \rightarrow C &= Y(1 + \frac{YZ}{4}) = (j6.66 \cdot 10^{-4}) \left(1 + \frac{(16 + j96)(j6.66 \cdot 10^{-4})}{4} \right) = \boxed{6.554 \cdot 10^{-4} \angle 90.16^\circ}
 \end{aligned}$$

(b)

$$\begin{aligned}
 V_{R,\phi} &= \frac{220}{\sqrt{3}} = 127.02 \text{ kV} \quad S_{3\phi} = \frac{250}{0.99} = 252.53 \text{ MVA} \\
 \rightarrow I_R &= \frac{S_{3\phi}}{\sqrt{3}V_{R,LL}} = \frac{252.53 \cdot 10^6}{\sqrt{3}(220 \cdot 10^3)} \angle (-\cos^{-1}(0.99)) = 662.8 \angle -8.11^\circ \text{ A} \\
 \rightarrow V_S &= AV_R + BI_R = (0.9681 \angle 0.317^\circ)(127.02 \cdot 10^3) + (16 + j96)(662.8 \angle -8.11^\circ) \\
 &= \boxed{155.3 \angle 23.6 \text{ kV}} \\
 \rightarrow I_S &= CV_R + DI_R = (6.554 \cdot 10^{-4} \angle 90.16^\circ)(127.02 \cdot 10^3) + (0.9681 \angle 0.317^\circ)(662.8 \angle -8.11^\circ) \\
 &= \boxed{635.6 \angle -0.35^\circ \text{ A}}
 \end{aligned}$$

(c)

$$\begin{aligned}
 V_{RFL} &= 127.02 \text{ kV}, \quad V_{RNL} = \frac{|V_S|}{|A|} = \frac{155.3}{0.9681} = 160.42 \text{ kV} \\
 \rightarrow \%VR &= \frac{V_{RNL} - V_{RFL}}{V_{RFL}}(100) = \frac{160.42 - 127.02}{127.02}(100) = \boxed{26.3\%}
 \end{aligned}$$

5.26

A 350-km, 500-kV, 60-Hz, three-phase uncompensated line has a positive-sequence series reactance $x = 0.34 \Omega/\text{km}$ and a positive-sequence shunt admittance $y = j4.5 \times 10^{-6} \text{ S/km}$. Neglecting losses, calculate: (a) Z_c , (b) γl , (c) the ABCD parameters, (d) the wavelength λ of the line in kilometers, and (e) the surge impedance loading in MW.

$$(a) \ Z_c = \sqrt{\frac{z}{y}} = \sqrt{\frac{j0.34}{j4.5 \cdot 10^{-6}}} = \boxed{274.87 \Omega}$$

$$(b) \ \gamma = \sqrt{zy} = \sqrt{(j0.34)(j4.5 \cdot 10^{-6})} = j1.237 \cdot 10^{-3} \text{ rad/km}$$

$$\rightarrow \gamma l = (j1.237 \cdot 10^{-3})(350) = \boxed{j0.4329 \text{ rad}}$$

(c)

$$A = D = \cosh(\gamma l) = \cos(0.4329) = \boxed{0.9078}$$

$$\rightarrow B = Z_c \sinh(\gamma l) = (274.87) \sinh(j0.4329) = j(274.87) \sin(0.4329) = \boxed{j115.3 \Omega}$$

$$\rightarrow C = \frac{1}{Z_c} \sinh(\gamma l) = \frac{j}{274.87} \sin(0.4329) = \boxed{j1.526 \cdot 10^{-3} \text{ S}}$$

$$(d) \ \lambda = \frac{2\pi}{\beta} = \frac{2\pi}{1.237 \cdot 10^{-3}} = \boxed{5080 \text{ km}}$$

$$(e) \ \text{SIL} = \frac{V_{LL}^2}{Z_c} = \frac{(500 \cdot 10^3)^2}{274.87} = \boxed{909.5 \text{ MW}}$$

5.27

Determine the equivalent π circuit for the line in Problem 5.26.

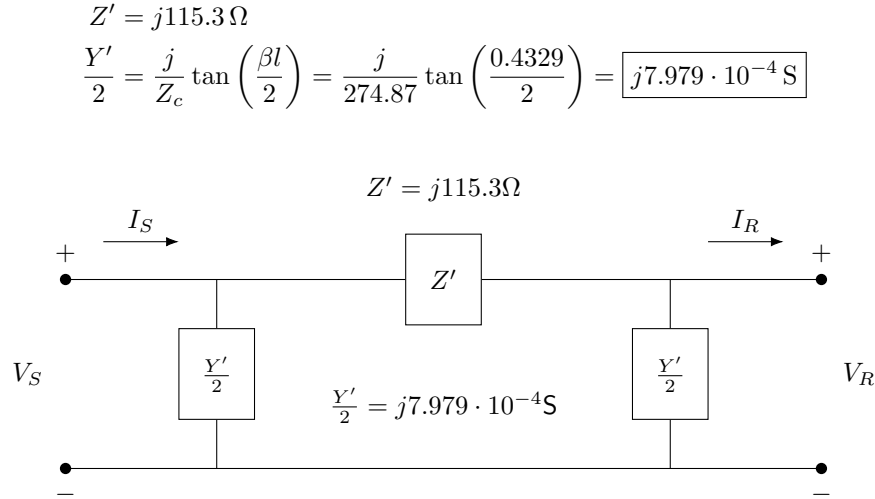


Figure 1: Equivalent π circuit for the transmission line in Problem 5.26.